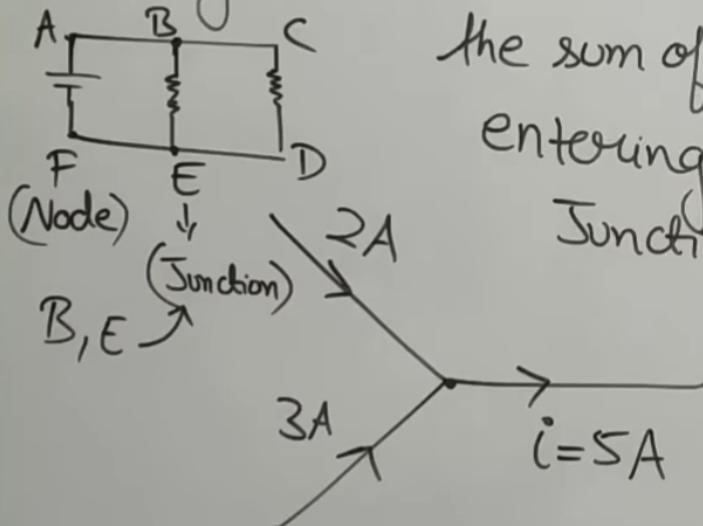


Kirchhoff's First Law / Junction Rule / Kirchhoff's

Current Law (KCL)

At any Junction,

where 3 or more wire/conductor
meets.




the sum of current
entering the
Junction

= Sum of current
Leaving the
Junction

$$4A \uparrow$$
$$3A \rightarrow$$
$$2A \rightarrow$$
$$i=5A \downarrow$$
$$3 + 4 = 2 + i$$
$$7 = 2 + i$$
$$\boxed{i = 5A}$$

Kirchhoff's 2nd Law / Loop Rule / Kirchhoff's Voltage Law (KVL)

Law (KVL)

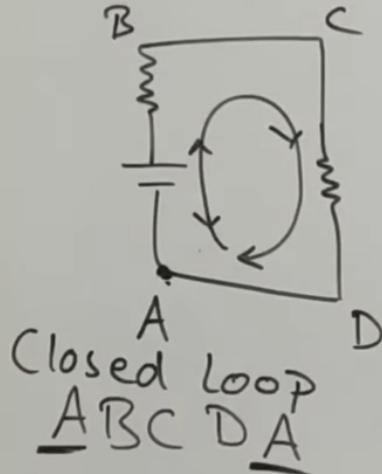

Closed Loop
A B C D A

$$V_A - V_A = 0$$

"The algebraic sum of change in potential around a CLOSED Loop is Zero."

$$\sum \Delta V = 0 \quad \text{Closed Loop.}$$

Potential gain $\rightarrow +V$ Potential drop $\rightarrow -V$

Closed Loop $\oint \pm V_1 \pm V_2 \pm V_3 \pm \dots \pm V_n = 0$

Principle of Conservation
of Energy.

KCL(Kirchoff's Current Law) is based on "**Conservation of Charge**"



Charge can neither be created nor be destroyed

Current is basically Charge per unit time

$$I = Q / t$$

KVL (Kirchoff's Voltage Law) is based on "**Conservation of Energy**"

Basically, $V = \frac{W_{ext}}{q}$




Work - joules / second

Thus, energy can neither be created nor be destroyed

How To Apply Kirchhoff's Law.

① Draw Current from one/more cell \rightarrow Svadanusari.

follow KCL for distribution of current.

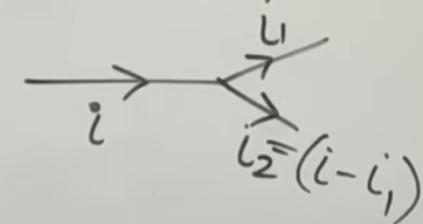


② Choosing a Loop.

i) Should be closed loop/loops.

Can involve any number of cells, resistors, capacitors etc.

③ Direction of Loop \rightarrow path.

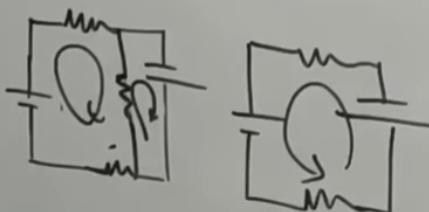

Clockwise / Anticlockwise.

2 loops in same questions \rightarrow take CW or ACW
one / both


How To Apply Kirchhoff's Law.

④ Potential drop or Potential gain.

Cells:



$$\Delta V = -\epsilon$$

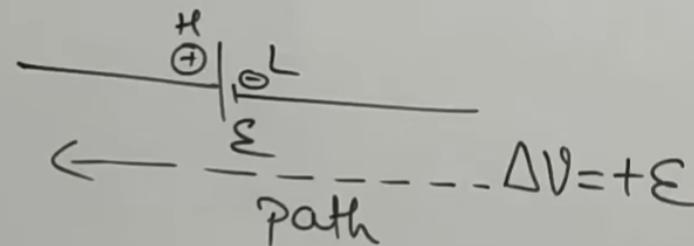


$$\Delta V = +\epsilon$$

Resistor.



$$\Delta V = -iR$$

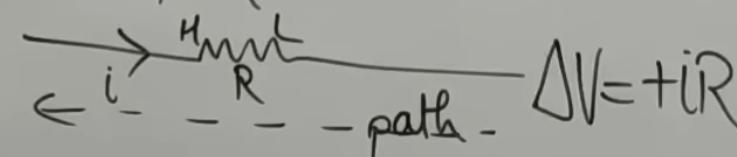

$$\Delta V = +iR$$

Higher Potential \rightarrow lower Potential

Potential drop

$$\Delta V = -ve$$

H \rightarrow L

Lower Potential \rightarrow Higher Potential

Potential gain

$$\Delta V = +ve$$


L \rightarrow H

***** Remember for KVL *****

In Cell, If Path follows from - to +, Take $\Delta V = +ve$

In resistors, If Current (i) and path are in opposite direction,
take $\Delta V = +ve$

Q1)

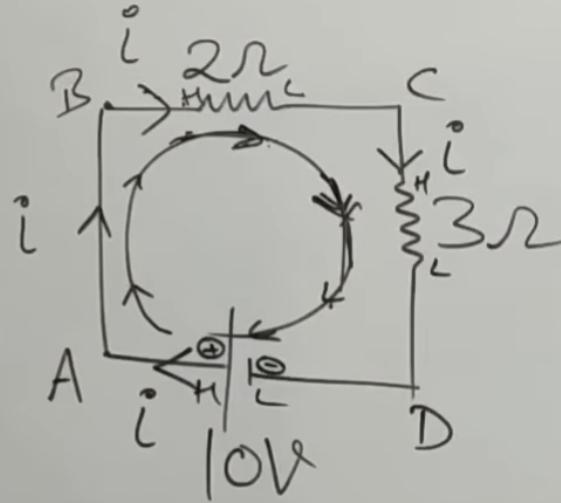

Loop ABCDA (Clockwise)


$$\sum \Delta V = 0$$

$$+10V - 2i - 3i = 0$$

$$5i = 10$$

$$i = \frac{10}{5} = 2A$$

(Q2)

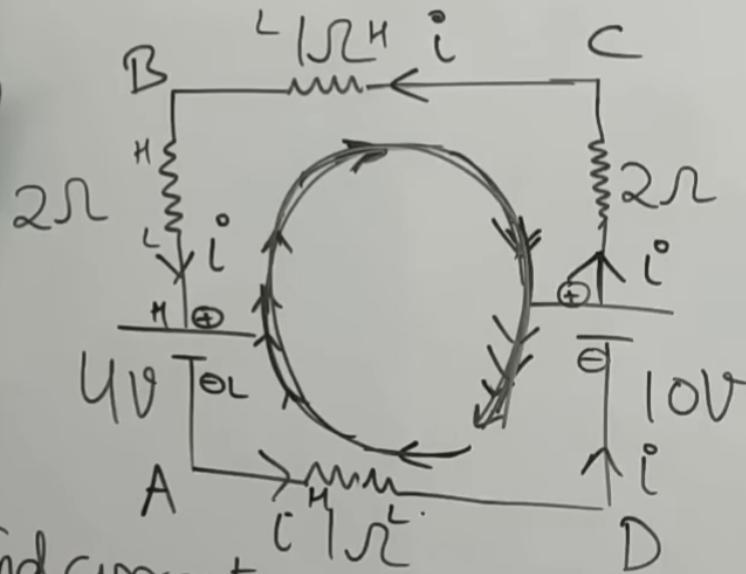

Find current
in each resistor.

Loop ABCDA (clockwise.)


$$\sum \Delta V = 0$$

$$+4V + 2i + 10V + i = 0$$

$$6i = 6$$

$$\boxed{i = 1A}$$


Q3)

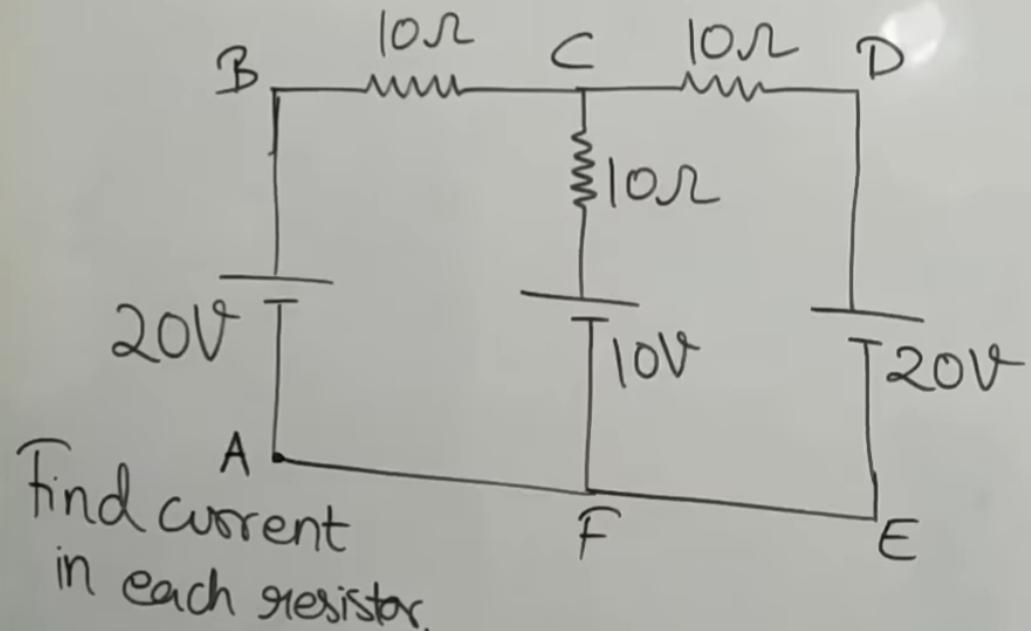

Find current
in each resistor.

Q3)

x.w.

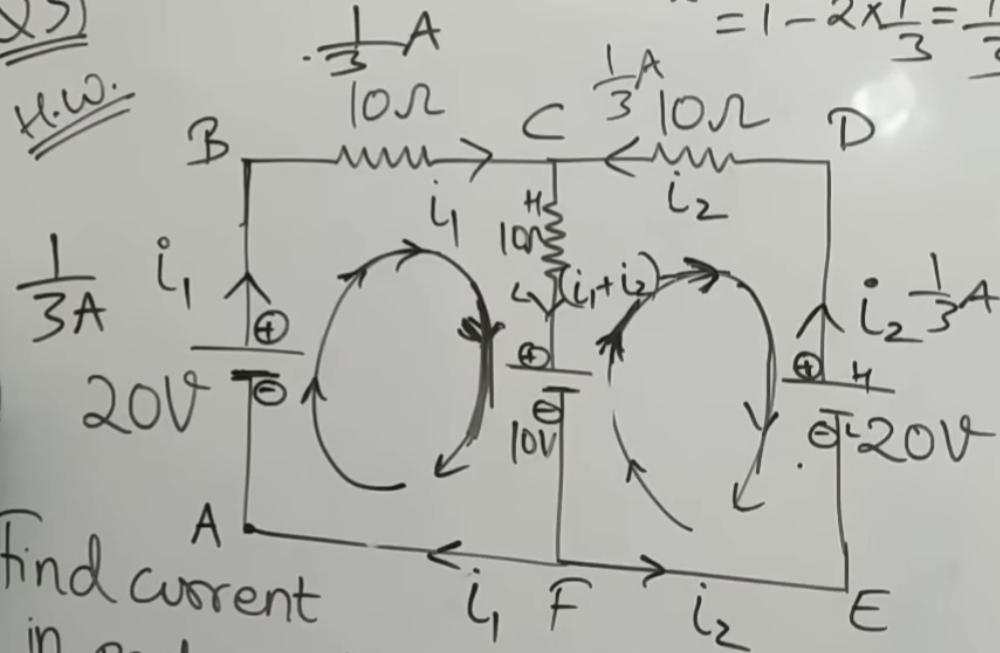

Find current
in each resistor.

Loop ABCFA

$$+20 - 10i_1 - 10(i_1 + i_2) - 10 = 0$$

$$\begin{aligned} i_2 &= 1 - 2i_1 \\ &= 1 - 2 \times \frac{1}{3} = \frac{1}{3}A \quad 20i_1 + 10i_2 = 10 \\ 2i_1 + i_2 &= 1 \quad (i) \end{aligned}$$

Loop CDEF

$$\begin{aligned} &+10 + 10(i_1 + i_2) \\ &+10i_2 - 20 = 0 \end{aligned}$$

$$20i_2 + 10i_1 = 10$$


$$2i_2 + i_1 = 1 \quad (ii)$$

$$\begin{array}{r} 2i_1 + i_2 = 1 \times 2 \\ 2i_2 + i_1 = 1 \\ \hline 3i_1 + 0 = 1 \end{array}$$

$$\begin{array}{l} 3i_1 = 1 \\ i_1 = \frac{1}{3} \end{array}$$

$$\text{Q3) } i = i_1 + i_2 = \frac{2}{3} - \frac{1}{3} = \frac{1}{3} A$$

x.W.

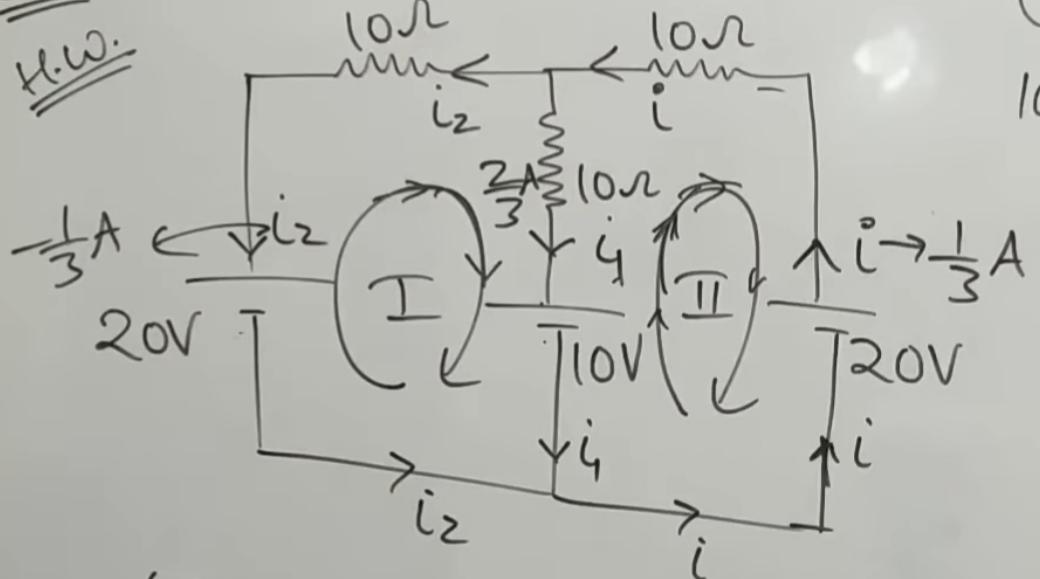

(I)

$$+20 + 10i_2 - 10i_1 - 10 = 0$$

$$10i_1 - 10i_2 = 10$$

$$i_1 - i_2 = 1$$

$$\begin{cases} \frac{2}{3} - i_2 = 1 \\ i_2 = \frac{2}{3} - 1 = -\frac{1}{3} \end{cases}$$

(II)

$$10 + 10i_1 + 10i - 20 = 0$$

$$10i_1 + 10i = 10$$

$$i_1 + i = 1$$


$$i_1 + i_1 + i_2 = 1$$

$$2i_1 + i_2 = 1$$

$$\begin{array}{r} i_1 - i_2 = 1 \\ \hline 3i_1 = 2 \end{array}$$

$$i_1 = \frac{2}{3} A$$

Ou) IIT 2015
Mains

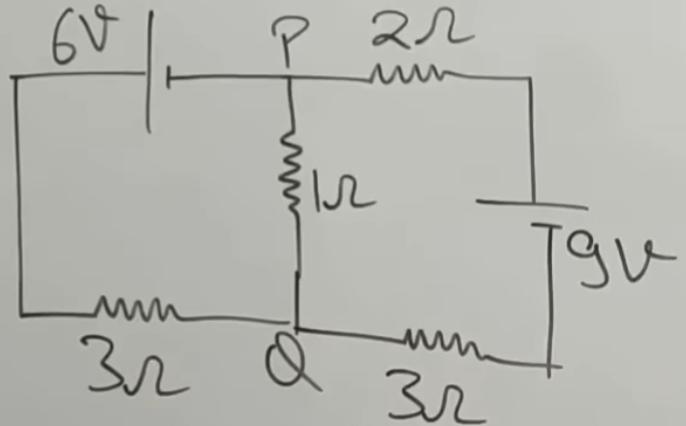


Find the current in
1Ω resistor.

- a) 1.13A P→Q
- b) 1.13A Q→P
- c) 0.13A Q→P
- d) 0.13A P→Q

OJU IIT 2015
Mains

$$i_1 = -\frac{3}{24} = \pm 0.125 A \approx -0.13 A$$

Loop ABPQA

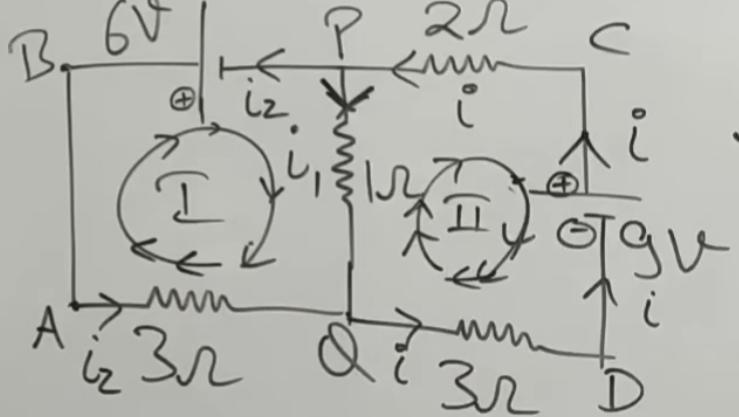

$$-6 - i_1 + 3i_2 = 0$$

$$\checkmark 3i_2 - i_1 = 6 - (i)$$

Loop PCDQP

$$-9 + 3i + i_4 + 2i = 0$$

Find the current in $i = i_1 + i_2$
1Ω resistor.

a) $1.13 A P \rightarrow Q$ $3i_2 - i_1 = 6 \times 5$

b) $1.13 A Q \rightarrow P$ $\checkmark 6i_1 + 5i_2 = 9 \times 3$

c) ~~$0.13 A Q \rightarrow P$~~ $\frac{-23i_4 = 3}{6i_1 + 5i_2 = 9}$ $\checkmark 6i_1 + 5i_2 = 9 - (ii)$

d) $0.13 A P \rightarrow Q$


$$5i + i_1 = 9$$

$$5(i_1 + i_2) + i_4 = 9$$

$$5i_1 + 5i_2 + i_4 = 9$$

$$\checkmark 6i_1 + 5i_2 = 9 - (ii)$$


Q6) IIT JEE
2017 Mains

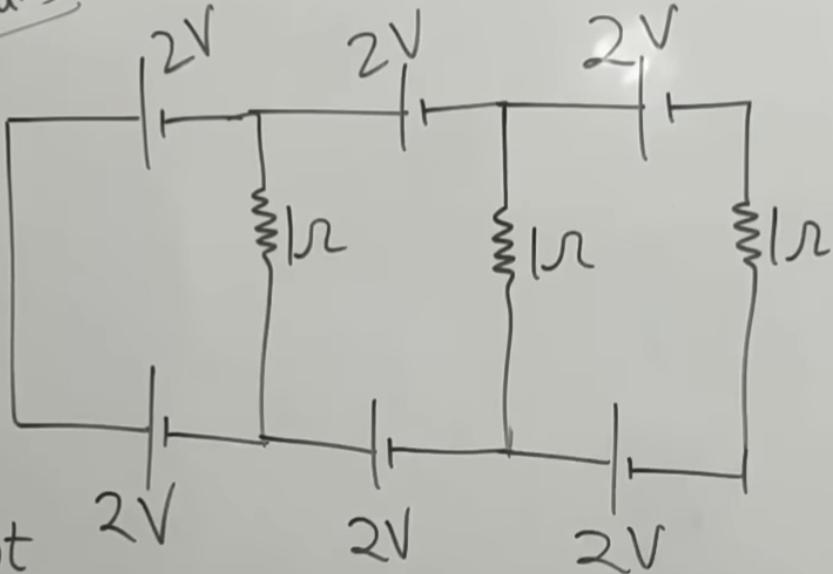

Find current in each resistor

- a) 0.25A
- b) 0.5A
- c) 0A
- d) 0.75A.

Q6) IIT JEE
2017 Mains

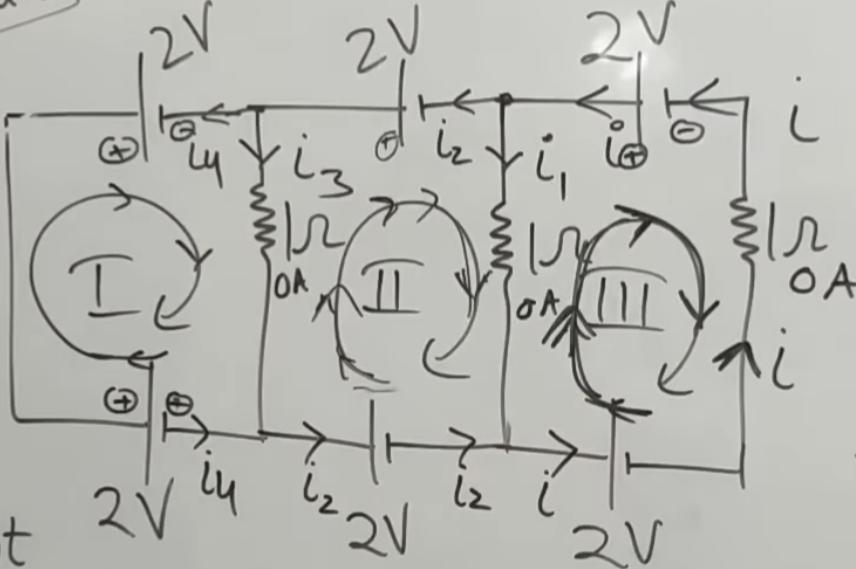

Find current
in each resistor

- a) 0.25A
- b) 0.5A
- c) 0.4
- d) 0.75A.

Loop I

$$+2V - 2V - i_3 \times 1 = 0$$

$$\boxed{i_3 = 0}$$

Loop II

$$+2V + i_3 - 2V$$

$$-i_1 = 0$$

$$\boxed{i_3 = i_1 = 0}$$


Loop III

$$+2V + i_1 - 2V$$

$$+i = 0$$


$$i = -i = 0$$

Q7)

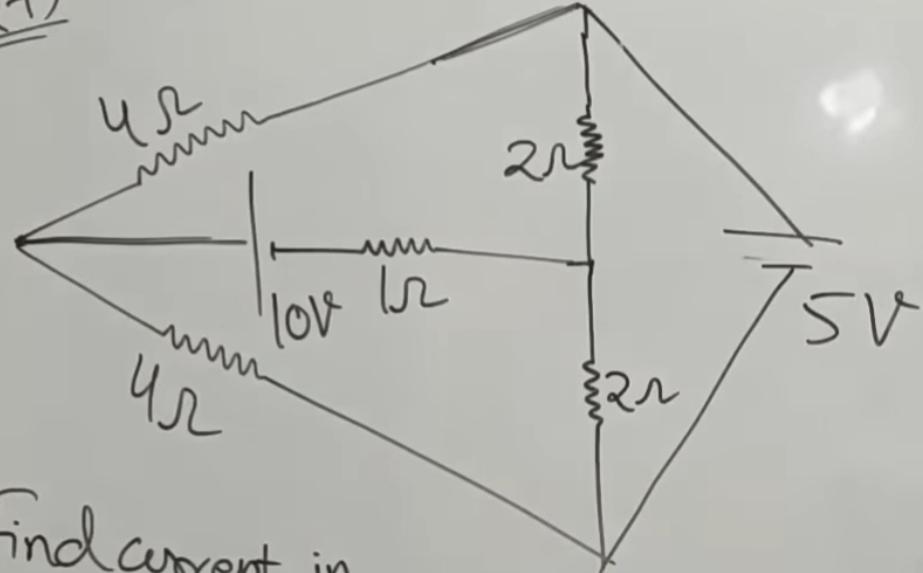

Find current in
each resistor.

Q7)

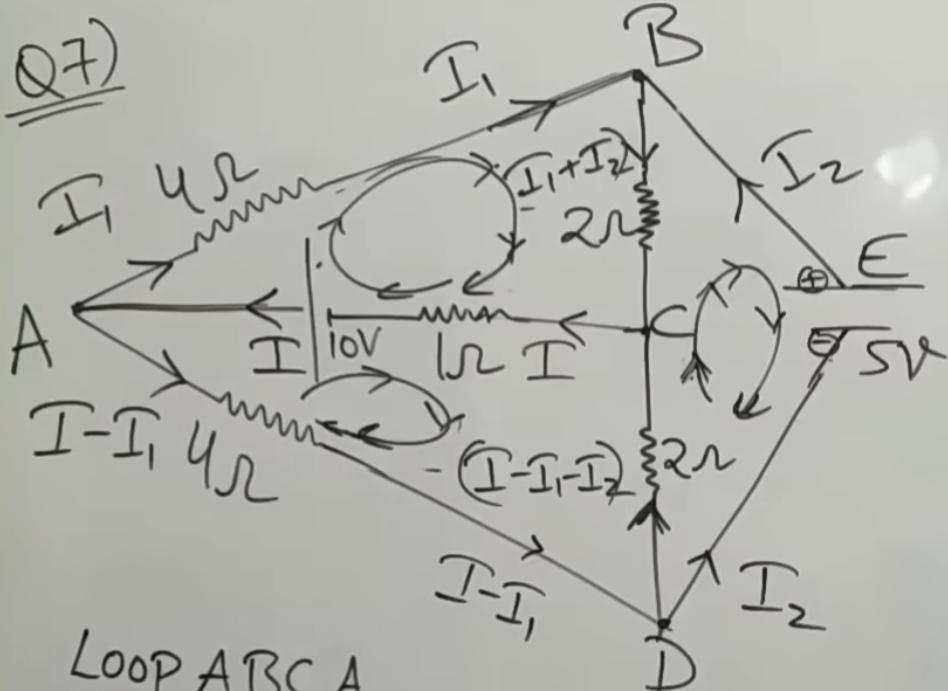

Loop ABCA

$$+10 - 4I_1 - 2(I_1 + I_2) - I = 0$$

$$I + 6I_1 + 2I_2 = 10 \quad (i)$$

Loop ACDA

$$\begin{aligned} -10 + I + 2(I - I_1 - I_2) \\ + 4(I - I_1) = 0 \end{aligned}$$

$$7I - 6I_1 - 2I_2 = 10 \quad (ii)$$

Loop III BEDB


$$\begin{aligned} -5 - 2(I - I_1 - I_2) \\ + 2(I_1 + I_2) = 0 \end{aligned}$$

$$4I_1 + 4I_2 - 2I = 5 \quad (iii)$$

$$I = 2.5A$$

$$I_1 = 0.625A$$

$$I_2 = 1.875A$$

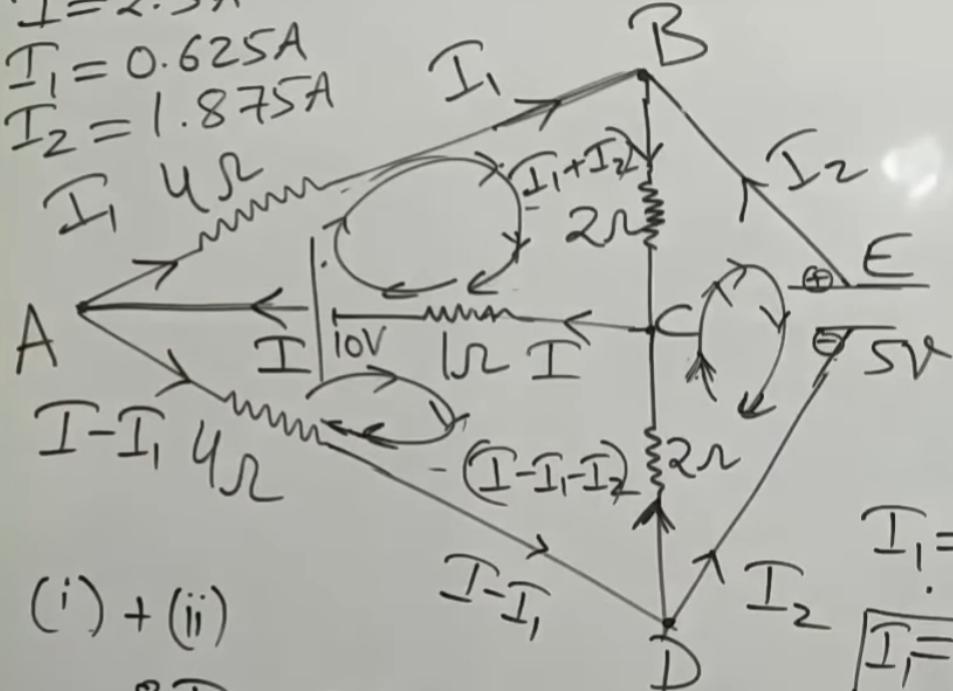

$$6I_1 + 2I_2 = 7.5 \times 2$$

$$\begin{aligned} & 4I_1 + 4I_2 = 10 \\ & 8I_1 + 0 = 5 \end{aligned}$$

$$7I - 6I_1 - 2I_2 = 10 - (ii)$$

$$I_1 = \frac{5}{8}$$

$$\boxed{I_1 = 0.625A}$$

$$4I_1 + 4I_2 - 2I = 5 - (iii)$$


$$36 \times \frac{5}{8} + 2I_2 = \frac{15}{2}$$

$$2I_2 = \frac{15}{2} - \frac{15}{4}$$

$$\boxed{I_2 = \frac{15}{8}}$$


Potential difference between 2 points.

$$V_A - V_B = ?$$

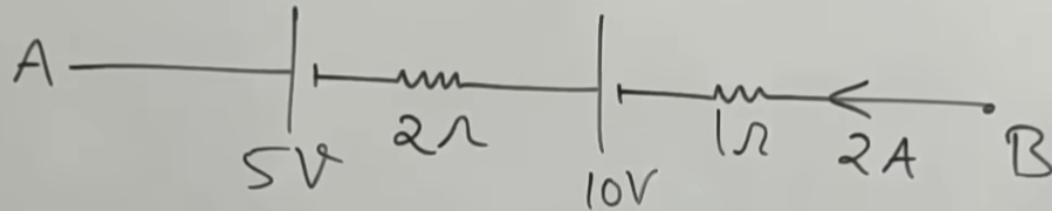

Potential difference between 2 points.

$$V_A - V_B = 8V.$$

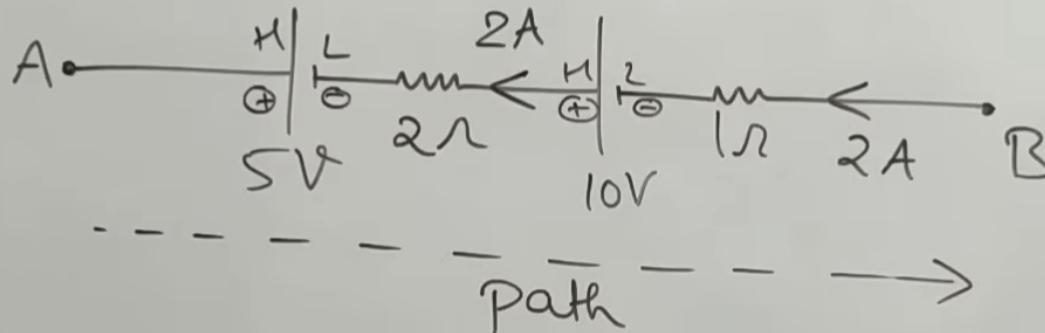


$$V_A - 5 + 2 \times 2 - 10 + 1 \times 2 = V_B$$

$$V_A - 8 = V_B$$

$$V_A - V_B = 8V$$

Potential difference between 2 points.

$$V_A - V_B = 8V.$$

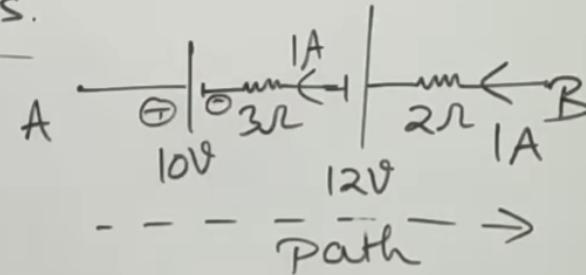


$$V_A - 10 + 3 \times 1 + 12 + 2 \times 1 = V_B$$

$$V_A + 7 = V_B$$

$$\boxed{V_A - V_B = -7V}$$

IIT
2011

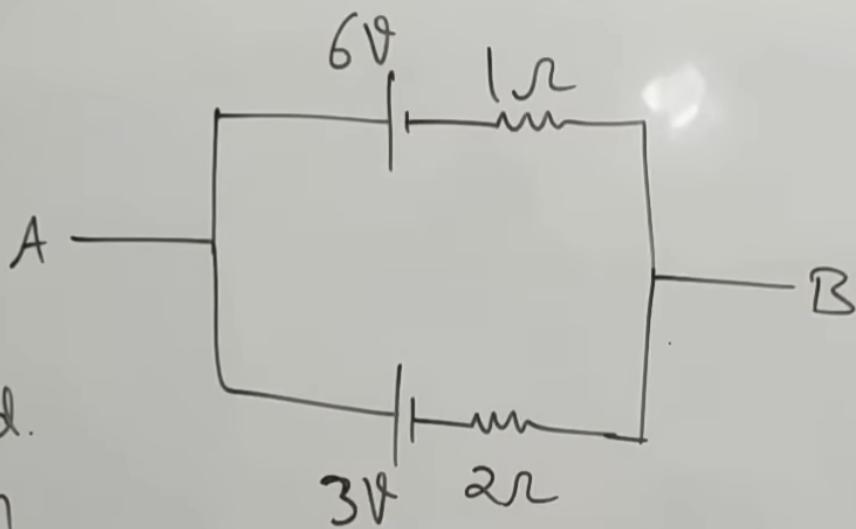


Find p.d.
between
A & B.

IIT
2011

Find p.d.
between
A & B.


$$V_A - 3 - 2 \times 1 = V_B$$

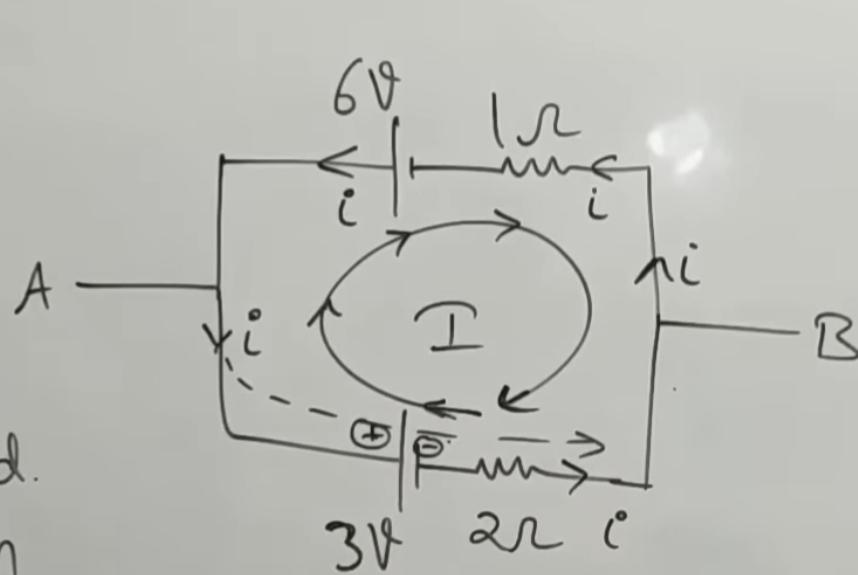

$$3V - 6V + i \times 1 + 2 \times i = 0$$

$$+3 = +3i$$

$$i = 1A$$

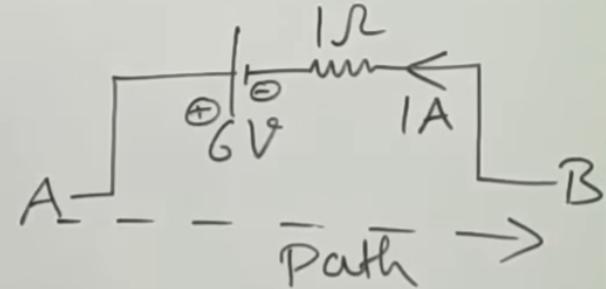

$$V_A - 6 + 1 \times 1 = V_B$$

$$V_A - 5 = V_B$$

$$V_A - V_B = 5V$$