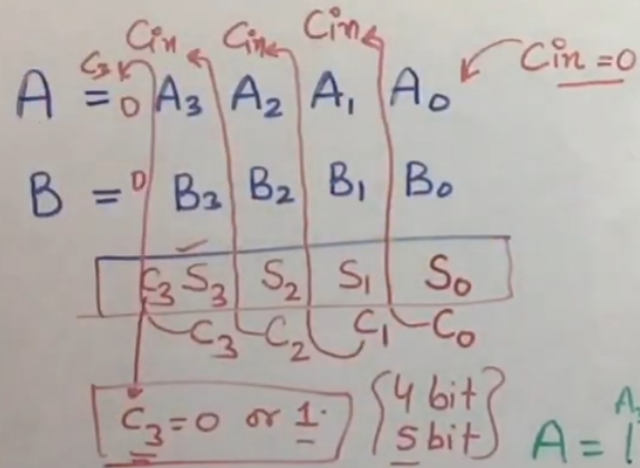


# Four Bit Parallel Adder using Full Adder




$$A = 1011 = 11$$

$$B = 1010 = 10$$

$$\begin{array}{r} 1011 \\ + 1010 \\ \hline 10101 \end{array}$$

Result:  $10101$  (21)

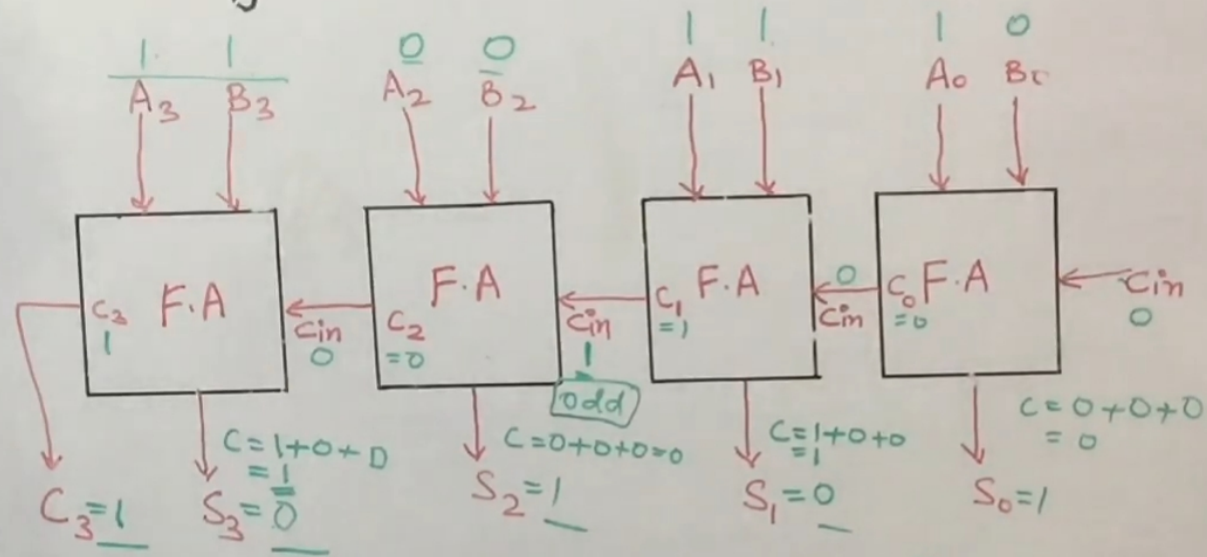

$$S = A \oplus B \oplus C$$

$$C = AB + BC_{in} + AC_{in}$$

Ex-or odd is detector  
Hige

$A = 1011 = 11$

$B = 1010 = 10$

$$\begin{array}{r} 1010 \\ 1010 \\ \hline 10100 \end{array}$$

$(21) \checkmark$

