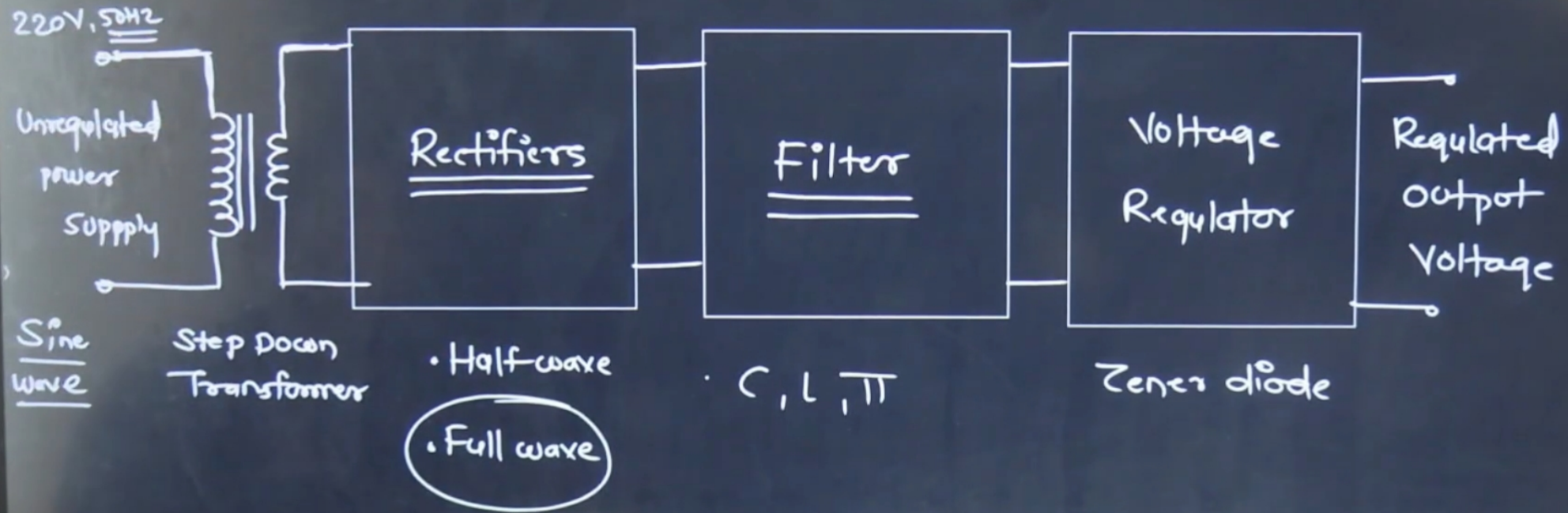



* Block Diagram of Regulated Power Supply

AC Transformers → Rectifier → Filter → Voltage Regulator → DC




Rectifier Circuits

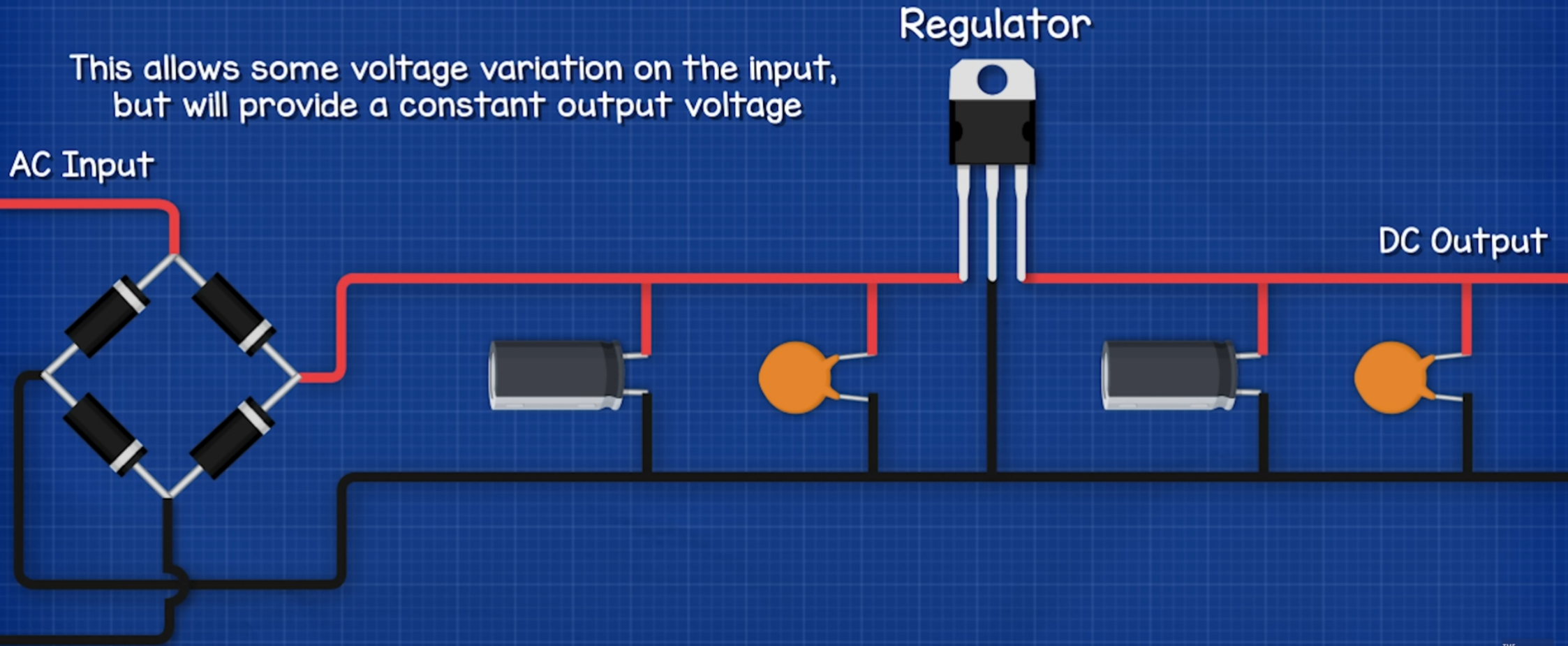
This allows some voltage variation on the input,
but will provide a constant output voltage




Unregulated AC
Input Voltage

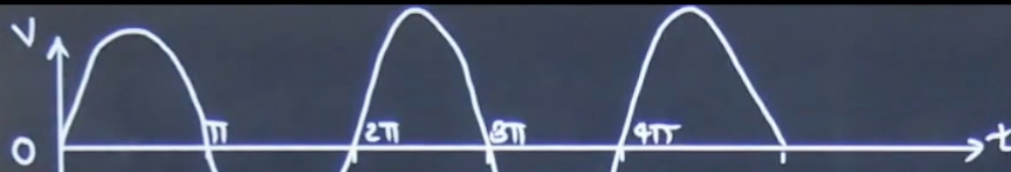


Transformer

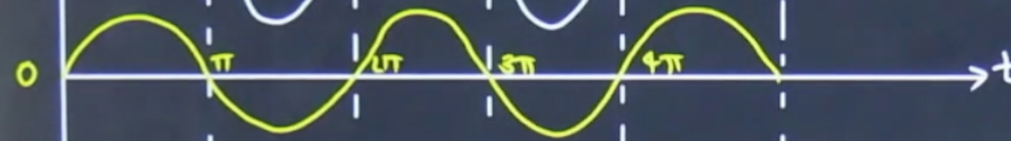

Rectifier

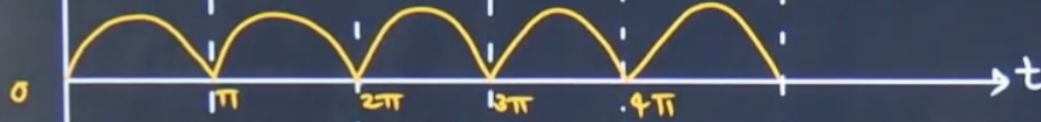

Filter

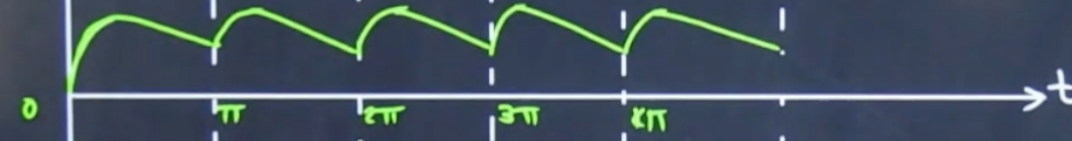

Voltage
Regulator

