

Designing Steps of a Combinational Circuit

Steps



1. Problem Definition.
2. The no. of available input Variables and required o/p variables is determined.
3. The I/P & o/p variables are assigned letter symbol.
4. Make a truth table to define the relationship between I/P & o/p
5. Get Simplified boolean function for each o/p is obtained.
6. Draw the logic diagram.



Steps of a Combinational Circuit

Prob: Design a combinational ckt with two I/Ps that produces high output when gives odd is I/P (1)

bles

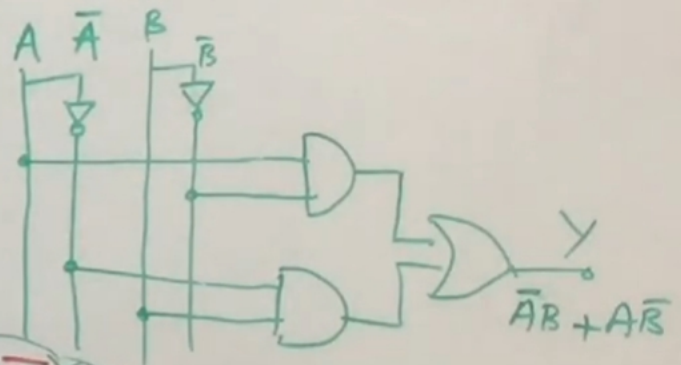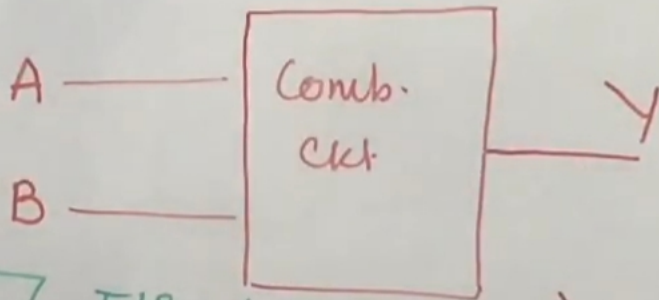

$2^n = 2^2 = 4$

I/Ps		O/P
A	B	Y
0	0	0
0	1	1 ✓
1	0	1 ✓
1	1	0

