

Problem Statement :-

PROBLEM :- Design a synchronous counter that has the following sequence

000, 010, 101, 110 and repeat

Step 1:-


No of FF = No. of Bits

3 FFs, D-Type FF

Step 2: Ext. D FF

Q_n	Q_{n+1}	$\check{D}$
0	0	0
0	1	1
1	0	0
1	1	1

Step 3: State Diagram

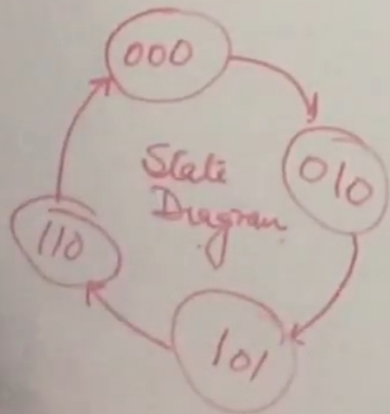

Excitation table & K-map for ckt :-

PS $Q_2 Q_1 Q_0$	NS $Q_2 Q_1 Q_0$	$D_2 D_1 D_0$		
0 0 0	0 1 0	0	1	0
0 0 1	X X X	X	X	X
0 1 0	1 0 1	1	0	1
0 1 1	X X X	X	X	X
1 0 0	X X X	X	X	X
1 0 1	1 1 0	1	1	0
1 1 0	0 0 0	0	0	0
1 1 1	X X X	X	X	X

$D_2 = Q_0 + \bar{Q}_2 Q_1$

$Q_2 Q_1$	00	01	11	10
0	0	1	0	X
1	X	X	X	1

$D_1 = Q_0 + \bar{Q}_1$

$Q_2 Q_1$	00	01	11	10
0	1	0	0	X
1	X	X	X	1

$D_0 = \bar{Q}_2 Q_1$

$Q_2 Q_1$	00	01	11	10
0	0	1	0	X
1	X	X	X	0

Final ckt for given problem :-

