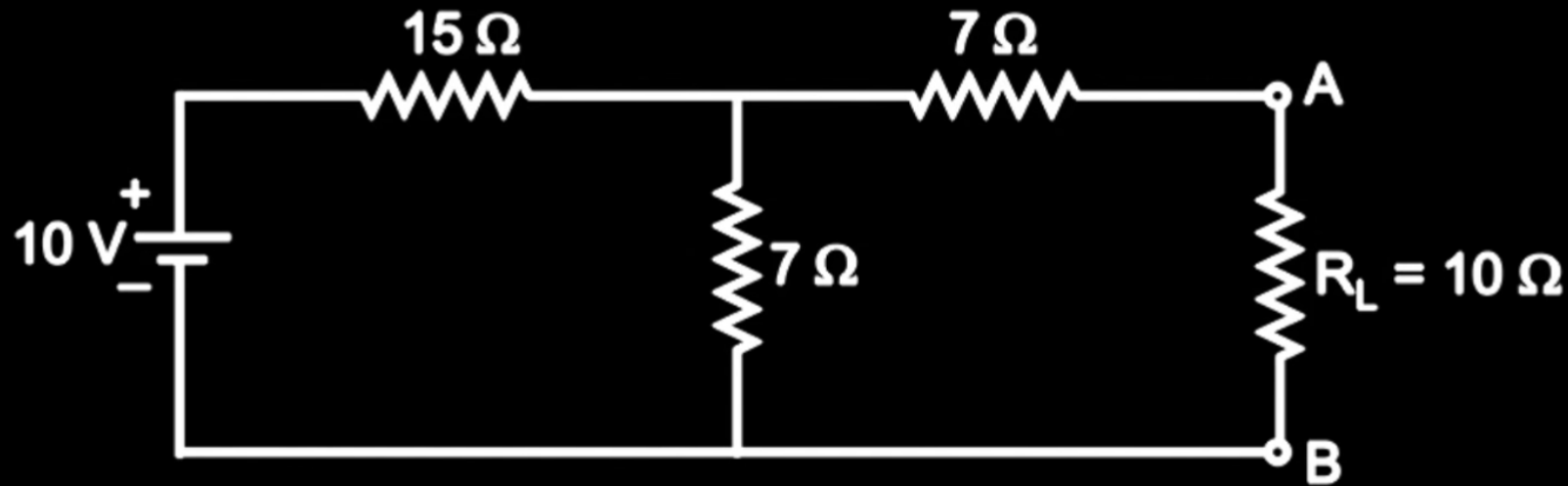



THEVENIN'S THEOREM [\(https://electrical-engineering.app/\)](https://electrical-engineering.app/)

Q. Develop Thevenin's equivalent circuit between the points A and B in Fig. and find current in $R_L = 10 \text{ Ohm}$.




Solution :

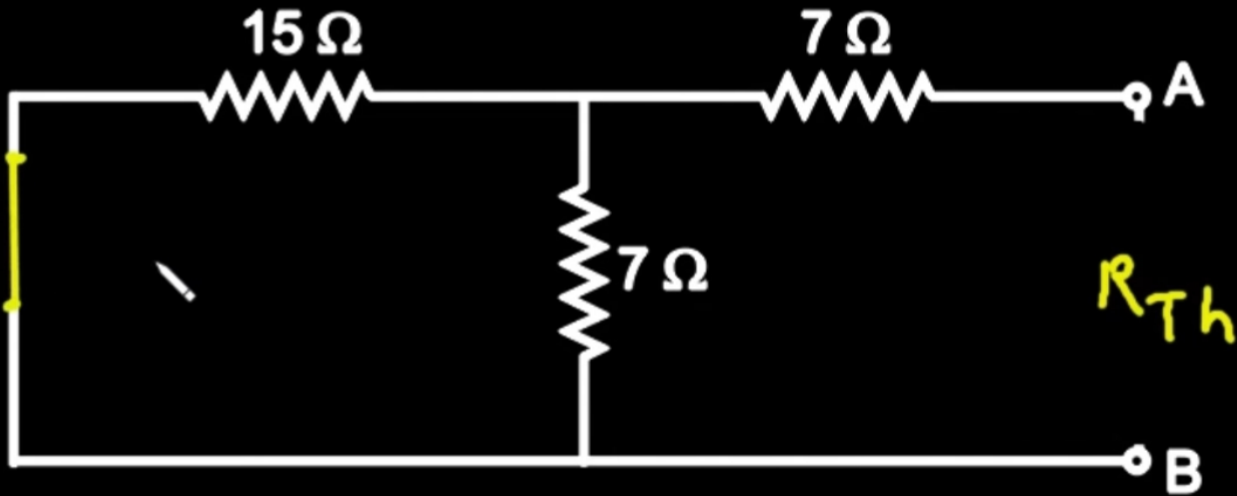① To find R_{Th} , Remove R_L & turn off all independent sources





INDEPENDENT SOURCE

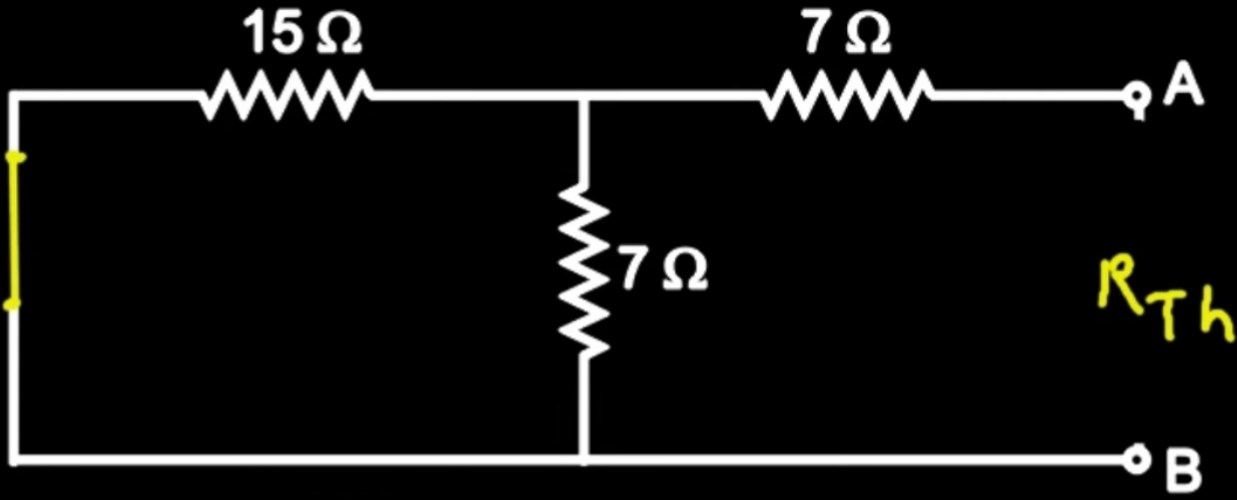

$$R_{Th} = 7 + \frac{15 \times 7}{15 + 7} = \frac{259}{22}\ \Omega$$

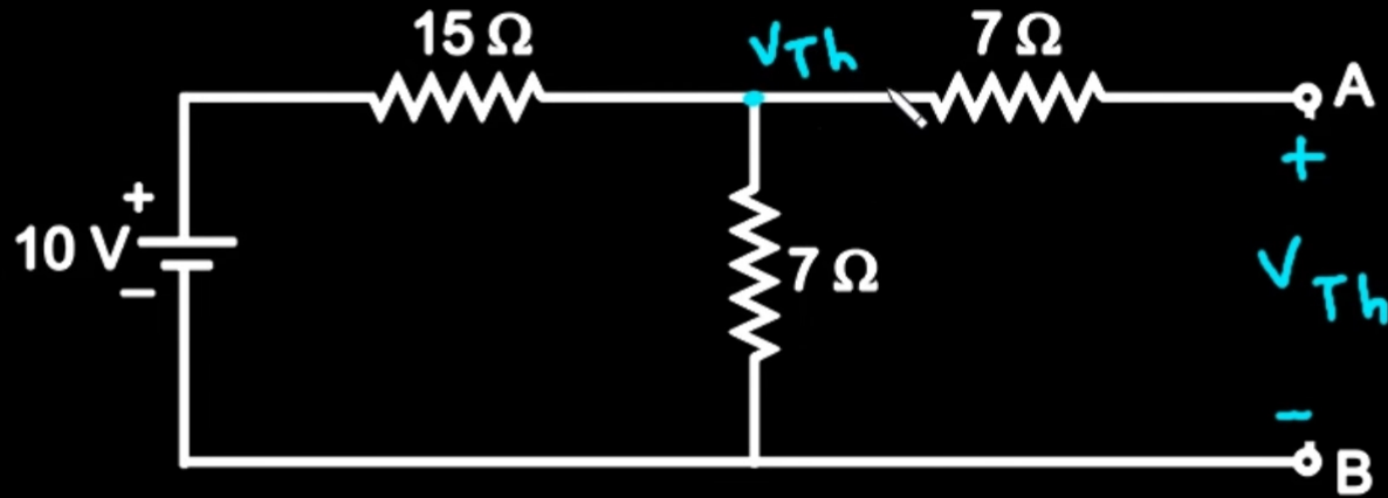② To find V_{Th} , Remove R_L & find V_{oc}



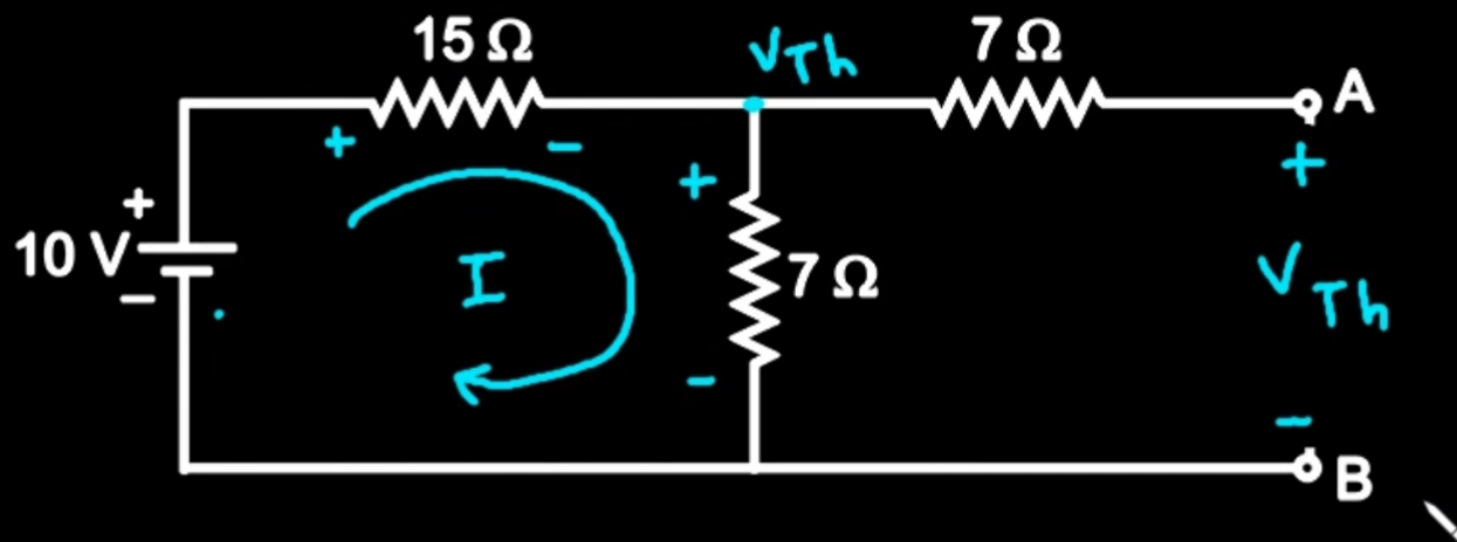

Apply KVL to loop

$$-10 + 15I + 7I = 0$$

$$-10 + 22I = 0$$

$$22I = 10$$

$$I = \frac{10}{22} \text{ A}$$

$$V_{Th} = 7 \times I = 7 \times \frac{10}{22} = \frac{35}{11} \text{ V}$$

$$V_{Th} = 3.181 \text{ V}$$

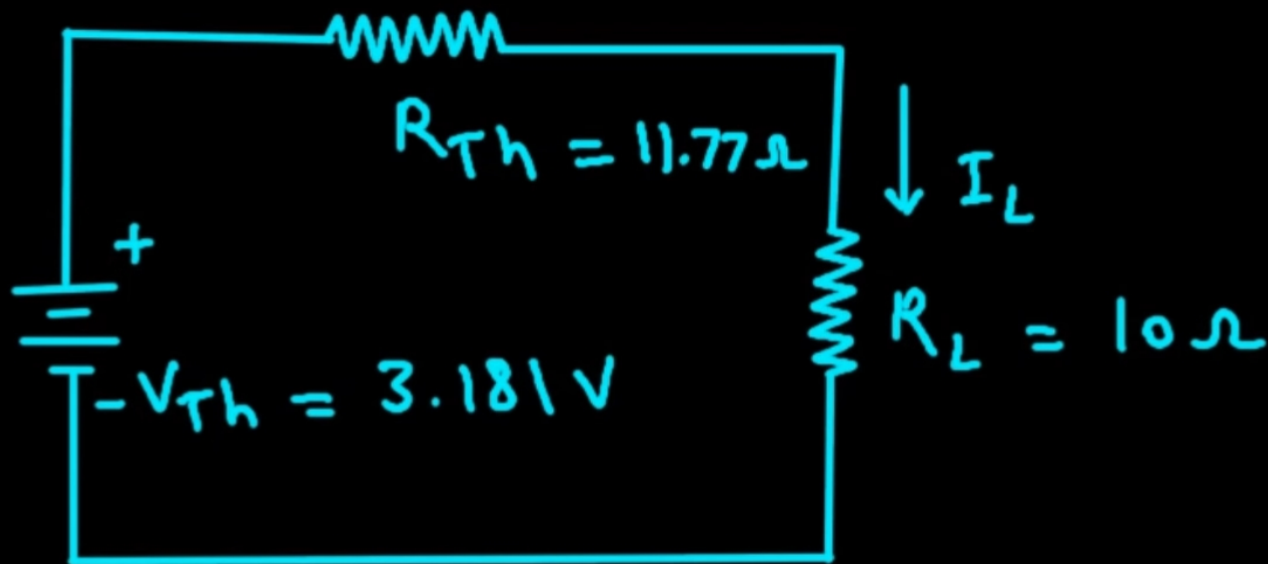


fig. Thevenin's equivalent circuit

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{3.181}{11.77 + 10} = 0.146 \text{ A}$$