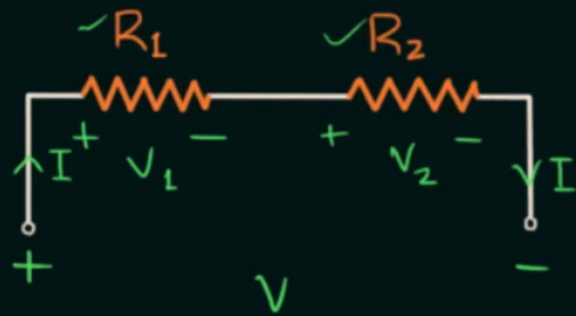


Series $\rightarrow I \rightarrow$ Same



$$R_{eq} = R_1 + R_2$$


$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2} \quad \text{total m.}$$

$$V_1 = IR_1 = \frac{V}{R_1 + R_2} \cdot R_1 \quad \text{own res.}$$

$$V_2 = IR_2 = \frac{V}{R_1 + R_2} \cdot R_2$$

$$V_3 = \frac{V}{R_1 + R_2 + \dots + R_n} \cdot R_3$$

Voltage Divider Rule

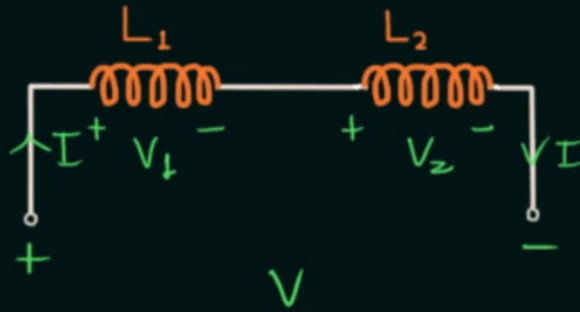


$$V = L_{eq} \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = \frac{V}{L_1 + L_2}$$


$$V_1 = L_1 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_1$$

$$V_2 = L_2 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_2$$
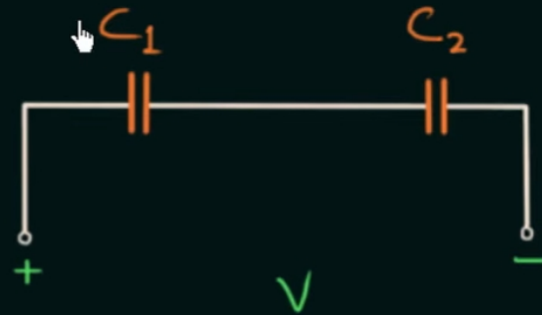
$$V_5 = \frac{V}{L_1 + L_2 + \dots + L_n} \cdot L_5$$



series $\rightarrow I \rightarrow$ same

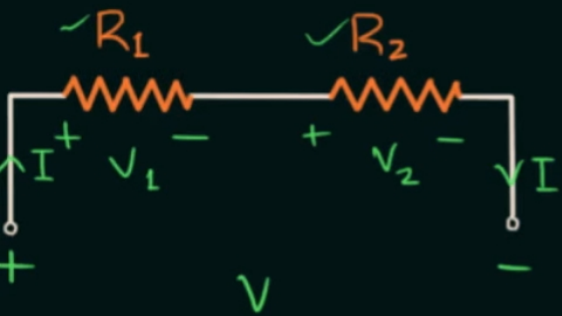

$$R_{eq} = R_1 + R_2$$

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2}$$


$$V_1 = IR_1 = \frac{V}{R_1 + R_2} \cdot R_1$$

total in.
 own
 del.

$$V_2 = IR_2 = \frac{V}{R_1 + R_2} \cdot R_2$$

$$V_n = \frac{V}{R_1 + R_2 + \dots + R_n} \cdot R_n$$

Voltage Divider Rule

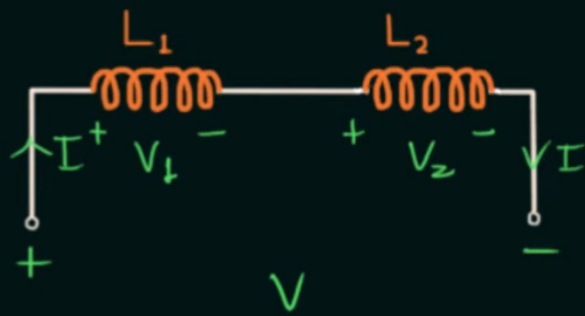


$$V = L_{eq} \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = \frac{V}{L_1 + L_2}$$

$$V_1 = L_1 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_1$$

$$V_2 = L_2 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_2$$
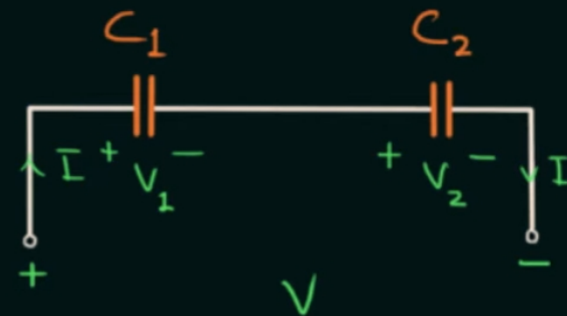
$$V_n = \frac{V}{L_1 + L_2 + \dots + L_n} \cdot L_n$$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


$$Q = C_{eq} V = \frac{C_1 C_2}{C_1 + C_2} \cdot V$$

$$V_1 = \frac{Q}{C_1} = \frac{C_1 C_2 V}{C_1 + C_2} \cdot \frac{1}{C_1} = \frac{V}{C_1 + C_2} \cdot C_2$$

$$V_2 = \frac{Q}{C_2} = \frac{V}{C_1 + C_2} \cdot C_1$$

How $V_3 = ?$

series $\rightarrow I \rightarrow$ same

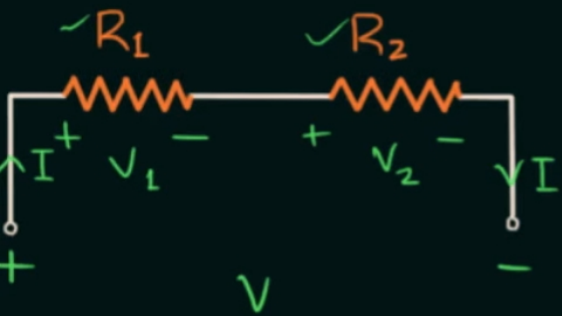

$$R_{eq} = R_1 + R_2$$

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2}$$


$$V_1 = IR_1 = \frac{V}{R_1 + R_2} \cdot R_1$$

total v.
own
del.

$$V_2 = IR_2 = \frac{V}{R_1 + R_2} \cdot R_2$$

$$V_n = \frac{V}{R_1 + R_2 + \dots + R_n} \cdot R_n$$

Voltage Divider Rule

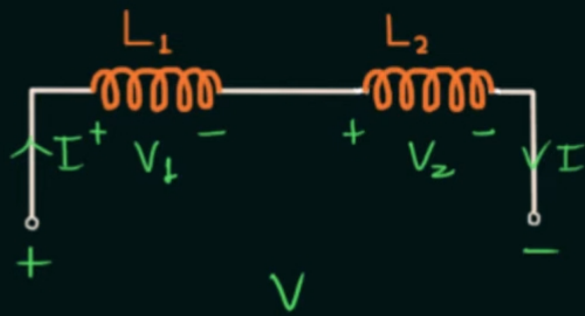


$$V = L_{eq} \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = \frac{V}{L_1 + L_2}$$

$$V_1 = L_1 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_1$$

$$V_2 = L_2 \frac{dI}{dt} = \frac{V}{L_1 + L_2} \cdot L_2$$
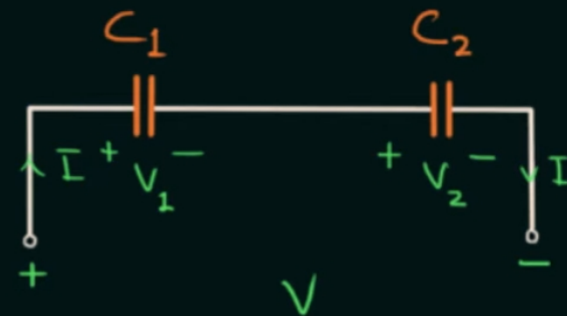
$$V_n = \frac{V}{L_1 + L_2 + \dots + L_n} \cdot L_n$$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$Q = C_{eq} V = \frac{C_1 C_2}{C_1 + C_2} \cdot V$$

$$V_1 = \frac{Q}{C_1} = \frac{C_1 C_2 V}{C_1 + C_2} \cdot \frac{1}{C_1} = \frac{V}{C_1 + C_2} \cdot C_2$$

$$V_2 = \frac{Q}{C_2} = \frac{V}{C_1 + C_2} \cdot C_1$$

How $V_3 = V_{Total} \cdot \frac{C_{eq}}{C_3}$

Do read this for Information on How to calculate Voltage through Capacitors with more than 2 capacitors :

<https://gemini.google.com/share/3ffa28f629a5>