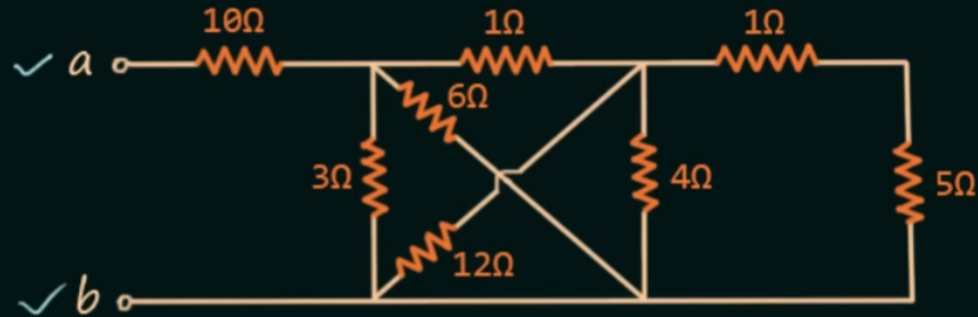


R_{eq}

Equivalent Resistance (Solved Problem 1)

Question: Find the equivalent resistance between the terminals a-b.




Solution:



R_{eq}

Equivalent Resistance (Solved Problem 1)

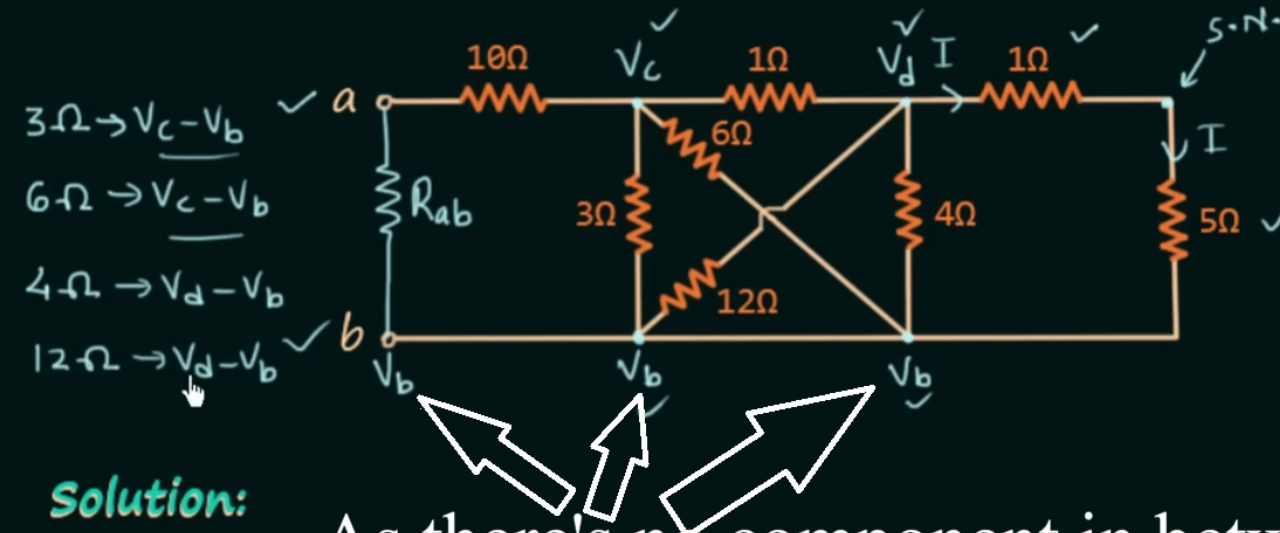Question: Find the equivalent resistance between the terminals a-b.



Solution:


As there's no component in between so all these **junctions** will have the same **Voltage V_b**



R_{eq}

Equivalent Resistance (Solved Problem 1)

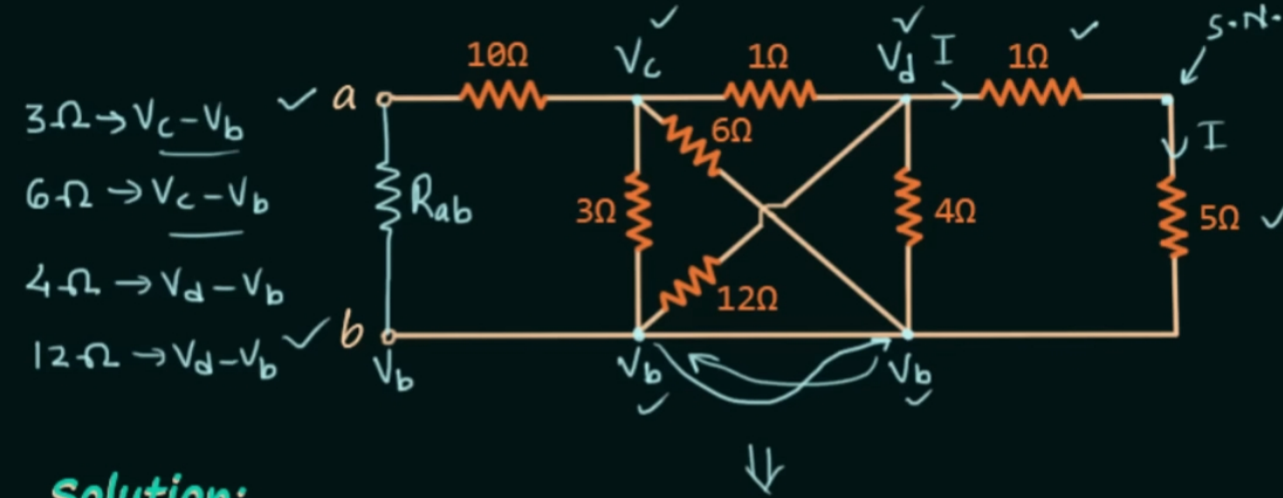Question: Find the equivalent resistance between the terminals a-b.



$$R_{ab} = (3 \parallel 6 + 1) \parallel 2 + 10$$


$$= \left(\frac{3 \times 6}{3 + 6} + 1 \right) \parallel 2 + 10$$

$$= 3 \parallel 2 + 10$$


$$R_{ab} = 6/5 + 10 \Rightarrow R_{ab} = 11.2\Omega$$

Ans


Solution:

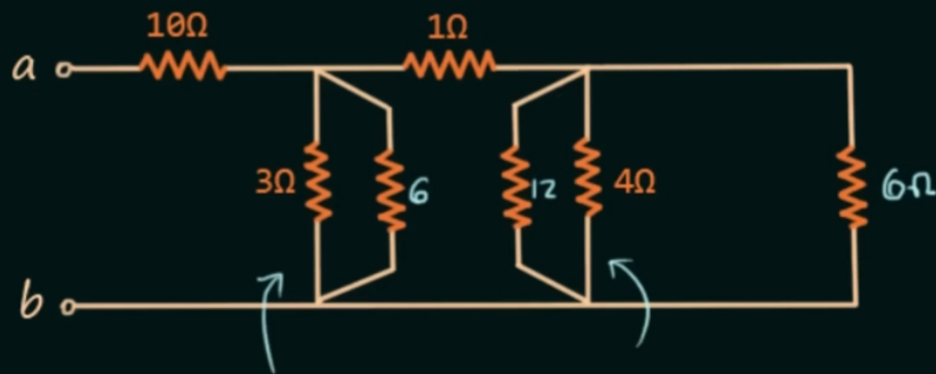

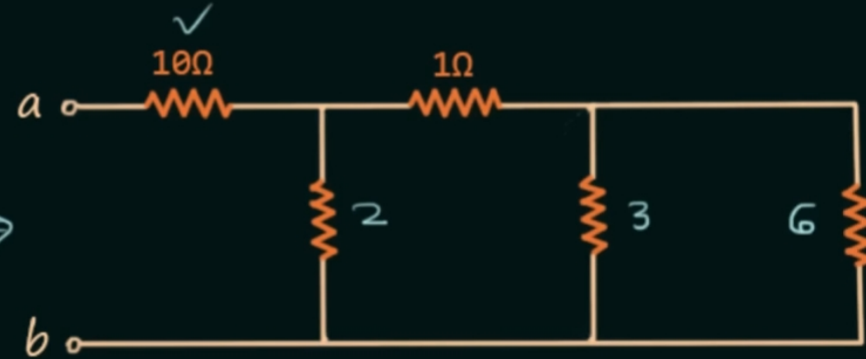
$$\checkmark \frac{3 \times 6}{3 + 6} = 2 \quad \checkmark \frac{12 \times 4}{12 + 4} = 3$$



Solution:

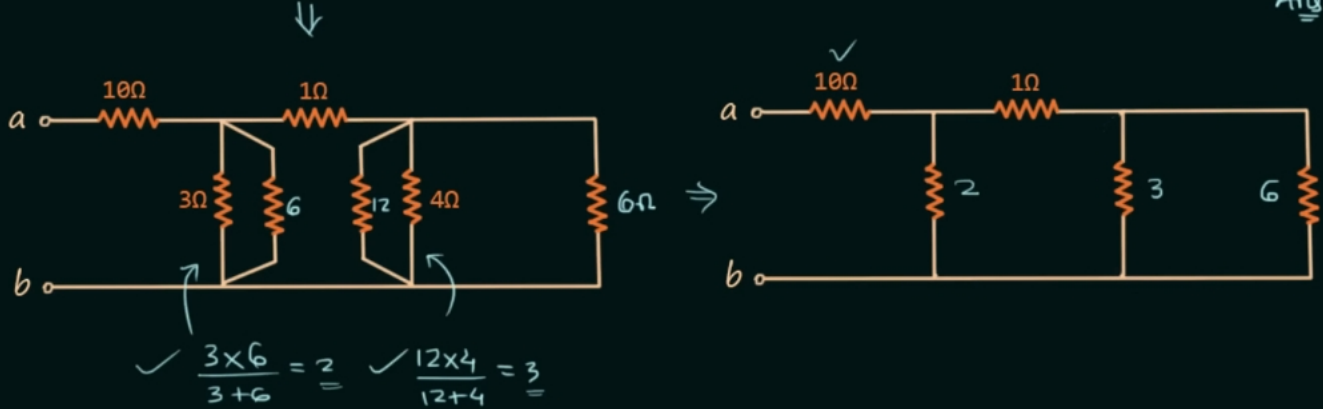


Homework:

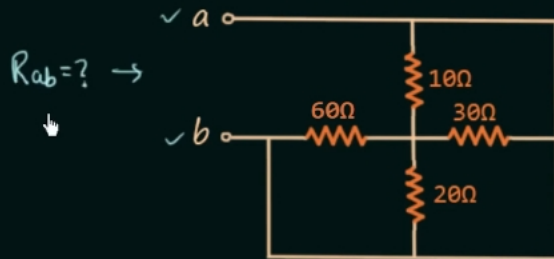

✓ Equivalent Resistance (Solved Problem 2)

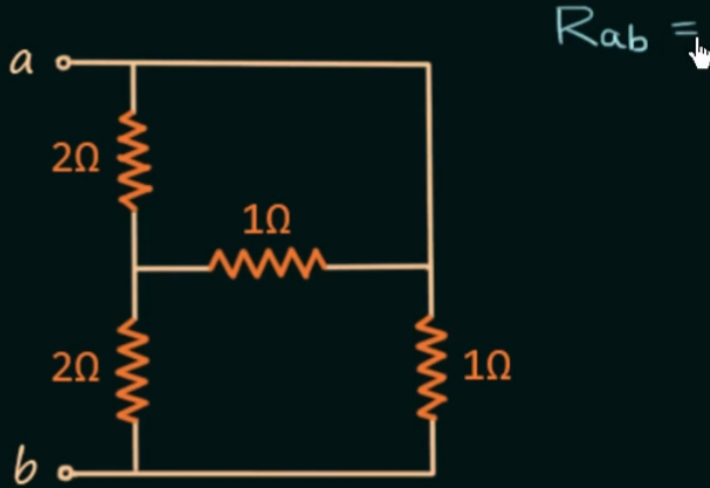Question: Find the equivalent resistance between the terminals a-b.




Solution:




✓ Equivalent Resistance (Solved Problem 2)

✓ Equipot. points

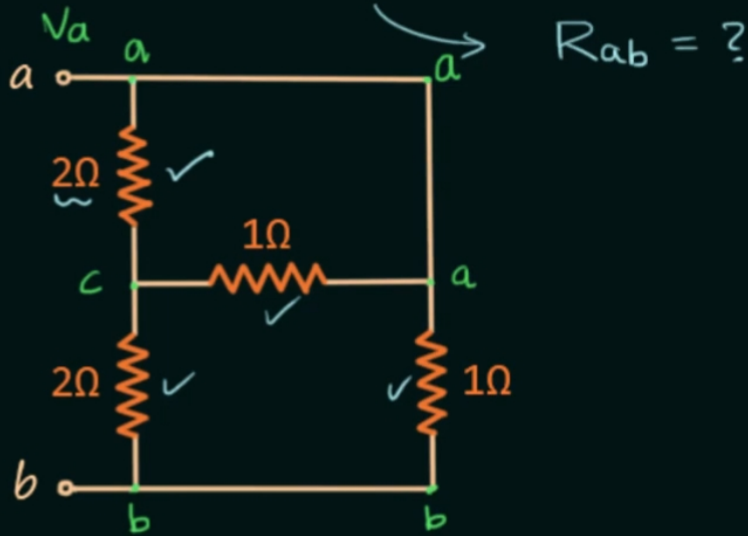Question: Find the equivalent resistance between the terminals a-b.



Solution:

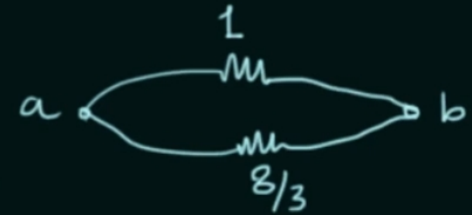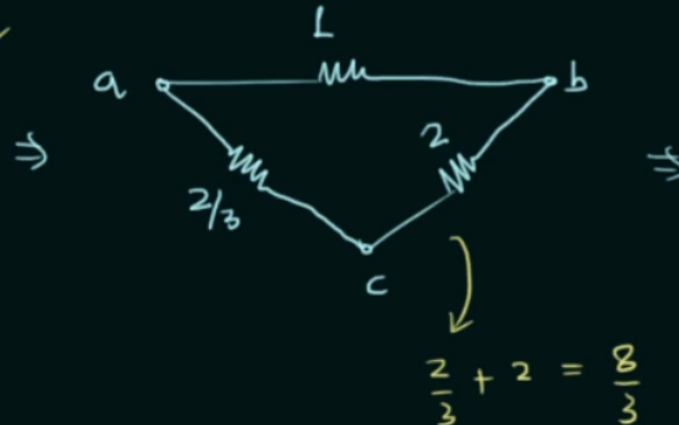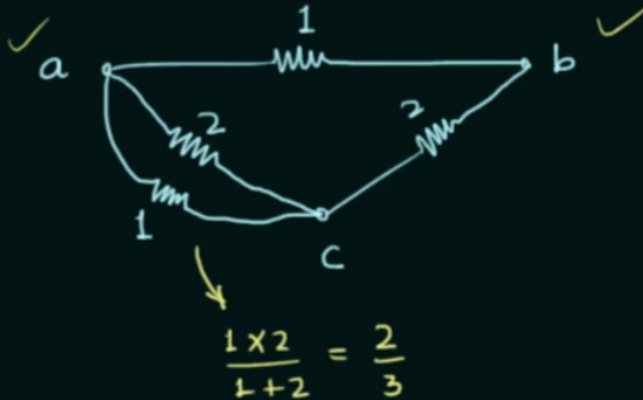

$$R_{ab} = \frac{1 \times \frac{8}{3}}{1 + \frac{8}{3}}$$

$$R_{ab} = 0.521 \text{ ohms} \\ = \frac{8}{11} \text{ ohms}$$

Homework:

R_{ab} $\rightarrow$

