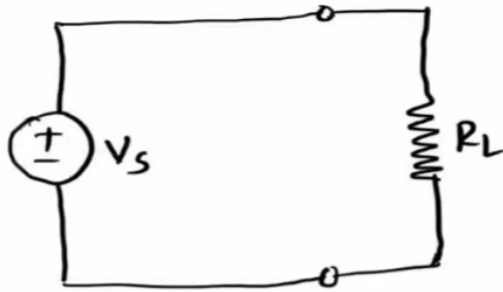



Ideal v/s. Practical Voltage Source :-



Ideal Voltage Source

→ It has zero internal resistance

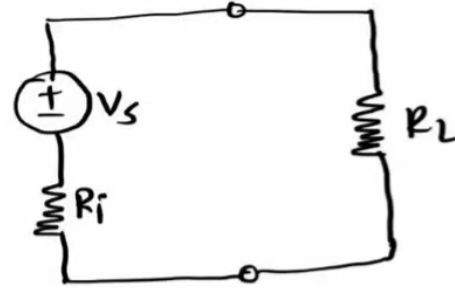
→ It delivers constant voltage across load R_L .




Practical Voltage Source.

→ It has R_i Internal resistance connected in series with voltage source.

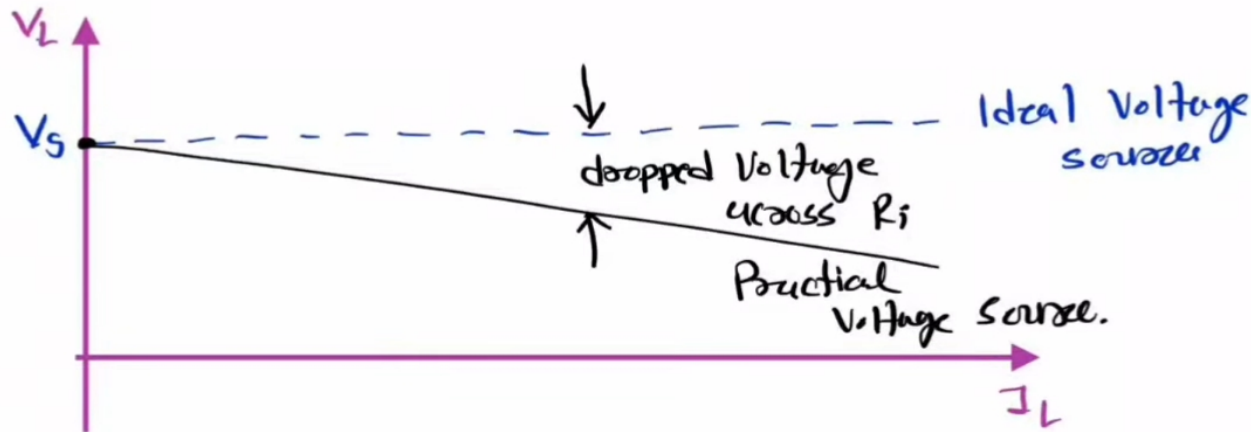
→ It has some voltage drop across R_i , so can not deliver V_s across load.



Ideal v/s. Practical Current Source :-

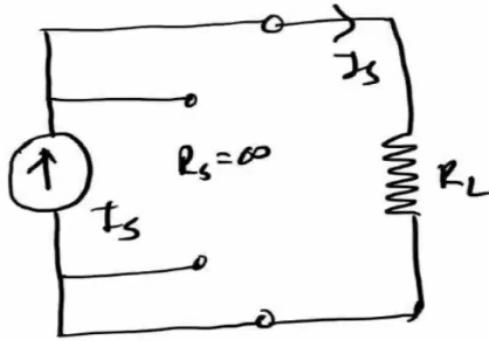

Ideal Current Source

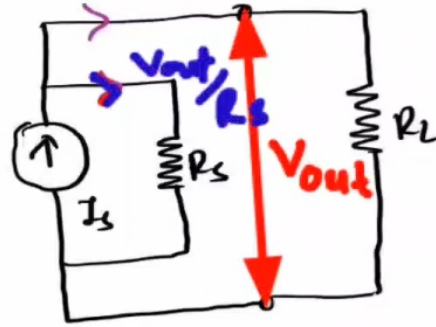

Practical Current Source

- It has infinite resistance in parallel across current source I_s
- It delivers constant current to load R_L
- It has finite resistance R_s connected in parallel to current source I_s .
- It can not give constant current to load as fractional current goes through R_s internal resistance.

