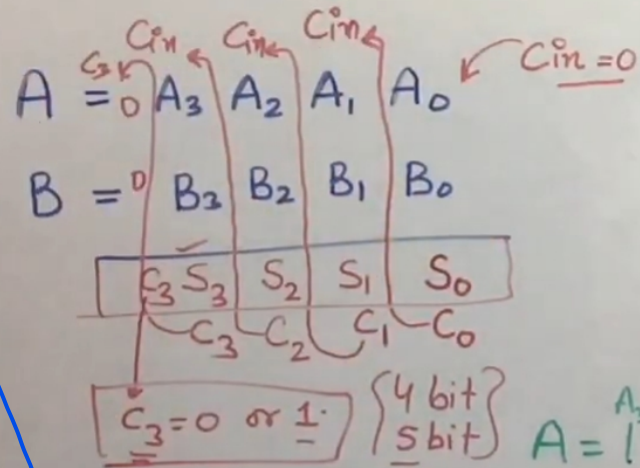


Four Bit Parallel Adder using Full Adder


IC - 74HC283



$$A = 1011 = 11$$

$$B = 1010 = 10$$
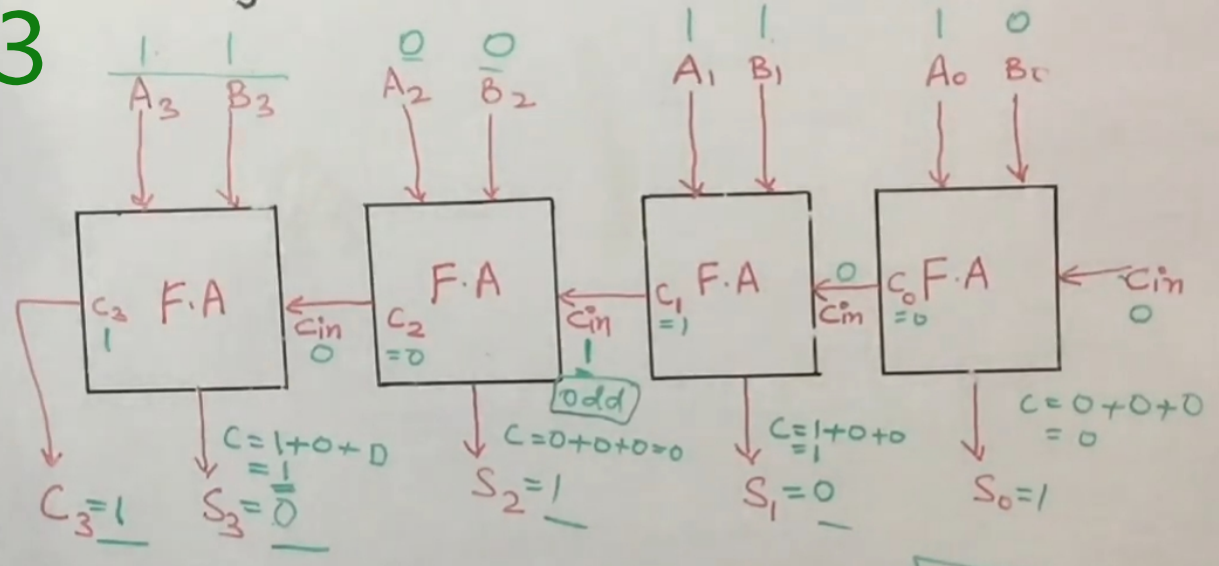
$$\begin{array}{r} 1011 \\ + 1010 \\ \hline 10101 \end{array}$$



$$S = A \oplus B \oplus C$$

$$C = AB + BC_{in} + AC_{in}$$

Ex-or odd is detector
Hige

Addition of Two 4-bit numbers

$$A = 1011 = 11$$

$$B = 1010 = 10$$

$$\begin{array}{r} 1010 \\ + 1011 \\ \hline 10101 \end{array}$$

(21) ✓

