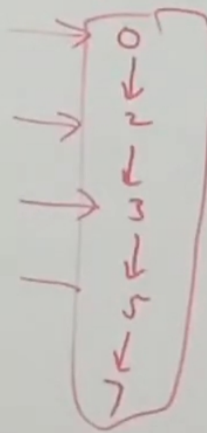



## SR FF Excitation Table

Prev.  
state

| S | R | $Q_{n+1}$ |
|---|---|-----------|
| 0 | 0 | 0         |
| 0 | 1 | 0         |
| 1 | 0 | 1         |
| 1 | 1 | 0         |



I/Ps  $\rightarrow$  Design



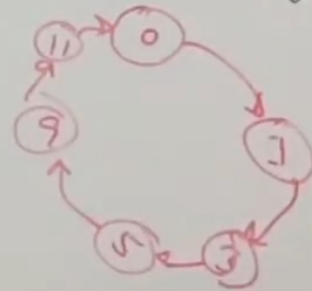


# SYNCHRONOUS COUNTER DESIGN

## JK FF excitation Table

| O/Ps  |           | I/Ps |   |   |   |
|-------|-----------|------|---|---|---|
| P S   | N S       | J    | K | J | K |
| $Q_n$ | $Q_{n+1}$ |      |   |   |   |
| 0     | 0         | 0    | 0 | 0 | X |
| 0     | 1         | 1    | 0 | 1 | X |
| 1     | 0         | 0    | 1 | X | 1 |
| 1     | 1         | 1    | 1 | X | 0 |

| J | K | $Q_{n+1}$   |
|---|---|-------------|
| 0 | 0 | $Q_n$       |
| 0 | 1 | 0           |
| 1 | 0 | 1           |
| 1 | 1 | $\bar{Q}_n$ |

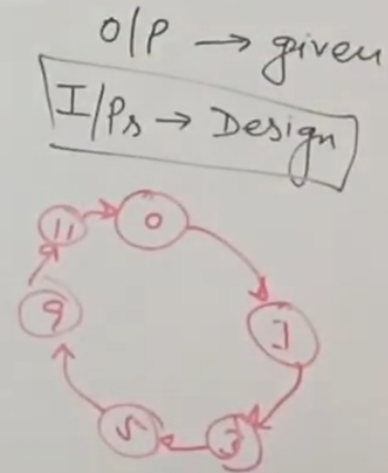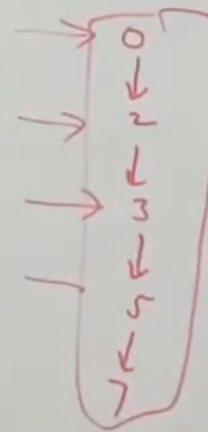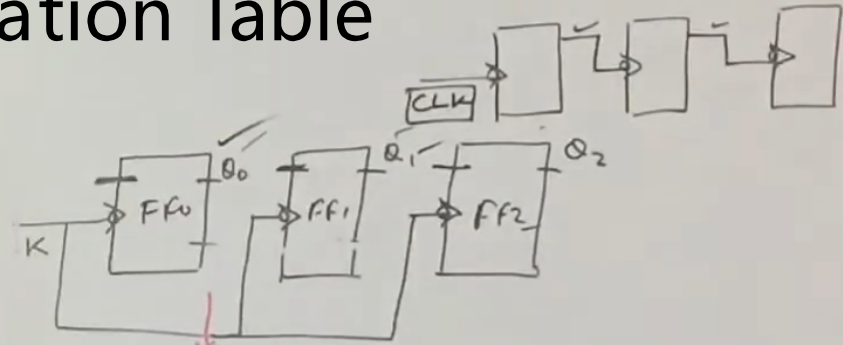

## D FF excitation Table

| T | $Q_{n+1}$        | D | $Q_{n+1}$ |
|---|------------------|---|-----------|
| 0 | $Q_n$            | 0 | 0         |
| 1 | $\overline{Q_n}$ | 1 | 1         |

