

SYNCHRONOUS COUNTER DESIGN

Step 1: Decide the no. & Type of Flip-Flops

Step 2: Excitation Table for the Flip-Flop

Step 3:- State Diagram & Ckt Exct. table

Step 4:- Obtain Boolean expression

Step 5:- Draw Ckt Diagram.



SYNCHRONOUS COUNTER DESIGN

Step 1: Decide the no. & Type of Flip-Flops

Step 2: Excitation Table for the Flip-Flop

Step 3: State Diagram & Ckt Exct. table

Step 4: Obtain Boolean expression

Step 5: Draw Ckt Diagram

Step 1: no. of FF = no. of Bits


2 FF $\rightarrow$ JK FF

ex: 2-Bit syn. Counter

Step 2: Excitation Table

PS	NS		
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


Step 3

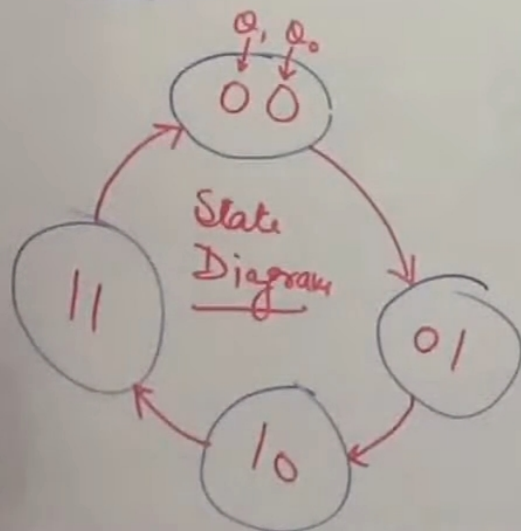

Step 4 : Excitation Table & K-map for ckt :-

0/Ps 1 1 X 0

Ps	N.S	I/P	
Q_1, Q_0	Q_1, Q_0	J_1, K_1	J_0, K_0
0 0	0 1	0	X
0 1	1 0	1	X
1 0	1 1	X	0
1 1	0 0	X	1

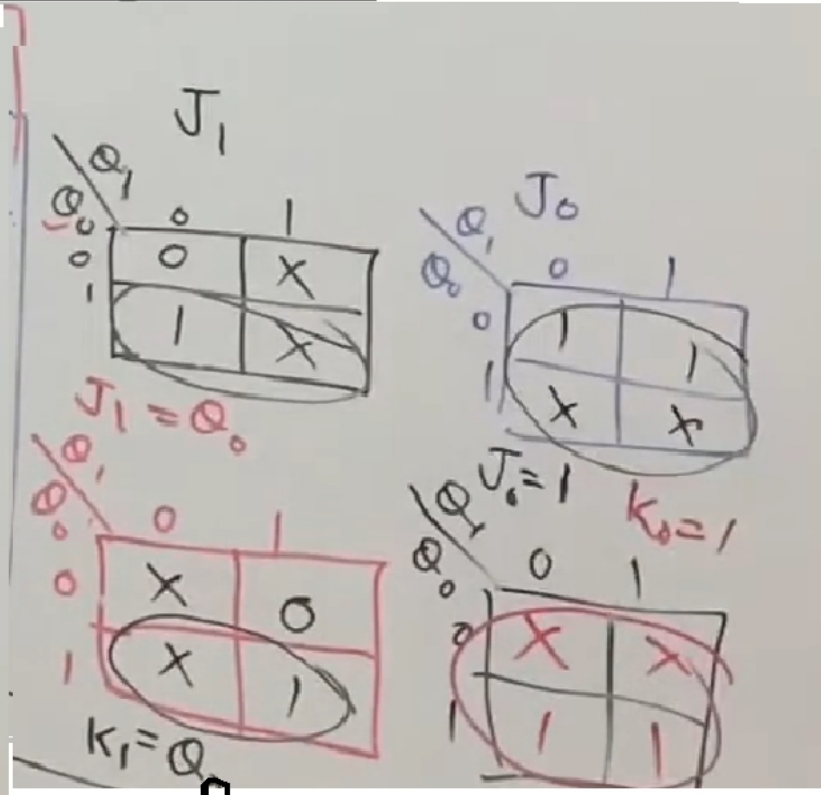

Final Ckt diagram for 2 bit Sync. Counter

